

ELEC ENG 2CF3

Assignment 6

**Voltage and Current Traveling Waves in
Transmission Line Equivalent Circuits**

Areeba Irfan - irfana20 - 400378045

April 7, 2023

EXERCISE 1: LOW-LOSS TRANSMISSION LINE

1. Include your MATLAB code.

```
%exercise 3 - Areeba Irfan - 400378045 - irfan20
clear all; close all %ok<CLALL> reset everything

%parameters based on student number
R = 1.8;
L = 286e-9;
G = 0.65e-3;
C = 115e-12;
F = 1,000,000,000;
W = F*(2*pi);

y = sqrt((R + i*W*L).*(G + i*W*C));
a = real(y);
b = imag(y);

Z = sqrt((R + i*W*L)./(G + i*W*C));
d = real(Z);
e = imag(Z);

vp = W/b;

%attenuation constant
subplot(5, 1, 1)
fplot(a, [1*F 10*F], 'green')
title("Attenuation Constant vs.Frequency") %title
xlabel('Frequency (GHz)');
ylabel('Attenuation');

%phase constant
subplot(5, 1, 2)
fplot(b, [1*F 10*F], 'magenta')
title("Phase Constant vs.Frequency")
xlabel('Frequency (GHz)');
ylabel('Phase Constant');

%phase velocity
subplot(5, 1, 3)
fplot(vp, [1*F 10*F], 'red')
title("Phase Velocity vs.Frequency")
xlabel('Frequency (GHz)');
ylabel('Phase Velocity [m/s]');

%the real part of characteristic impedance Z0
subplot(5, 1, 4)
fplot(d, [1*F 10*F], 'black')
```



```

title("Real Part of Characteristic Impedance vs.Frequency")
xlabel('Frequency (GHz)');
ylabel('Re [ohms]');


% the imaginary part of Z0
subplot(5, 1, 5)
fplot(e, [1*F 10*F], 'blue')
title("Imaginary Part of Characteristic Impedance vs.Frequency")
xlabel('Frequency (GHz)');
ylabel('Im [ohms]');

```

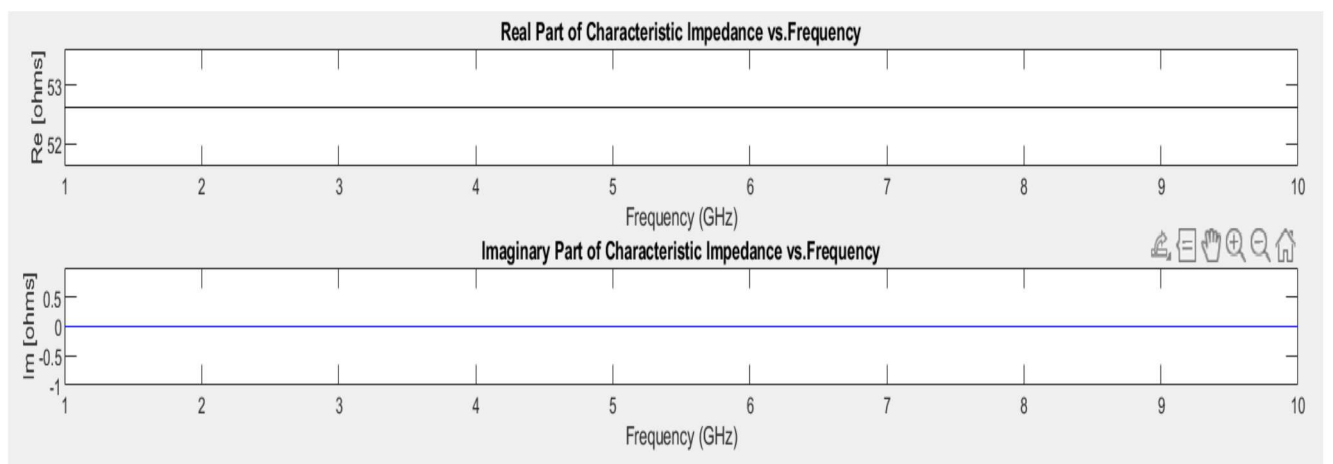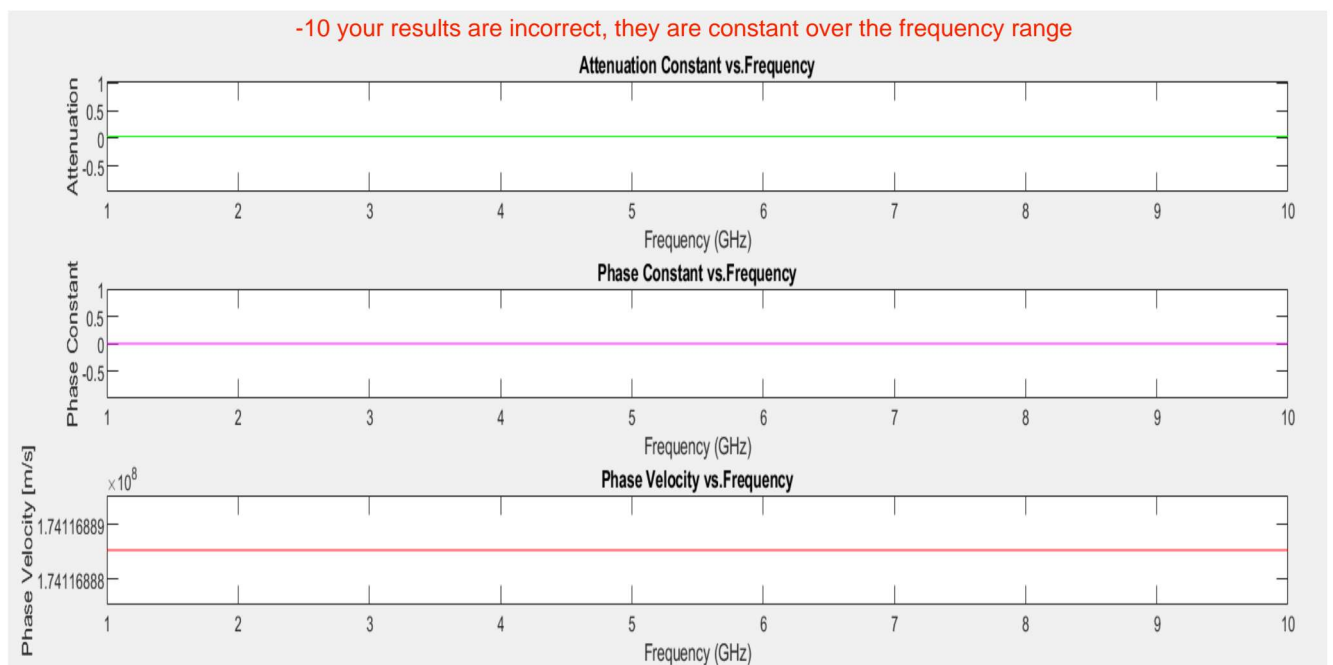2. Include the following MATLAB-generated plots



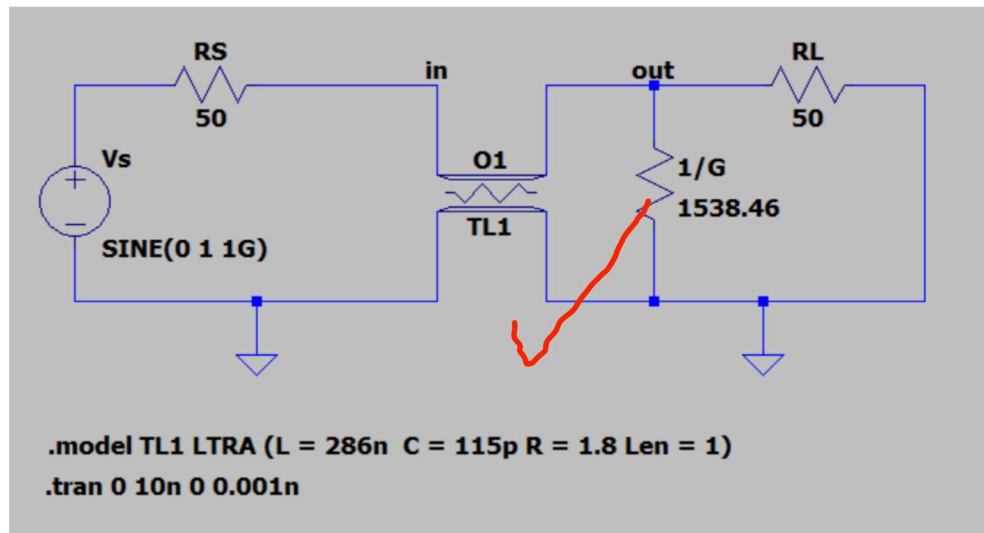3. Include the complete LTspice schematic




4. Include the complete LTspice netlist (View→SPICE Netlist).

```
* C:\Users\Areeba\Desktop\winter 2023\2EI4\Draft2.asc
O1 in 0 out 0 TL1
R$1/G out 0 1538.46
RL 0 out 50
RS in N001 50
Vs N001 0 SINE(0 1 1G)
.model TL1 LTRA (L = 286n C = 115p R = 1.8 Len = 1)
.tran 0 10n 0 0.001n
.backanno
.end
```

5. Include the LTspice (*.asc) file, named properly, e.g., Exercise1.asc.

The name of the file is exercise1_assignment 6

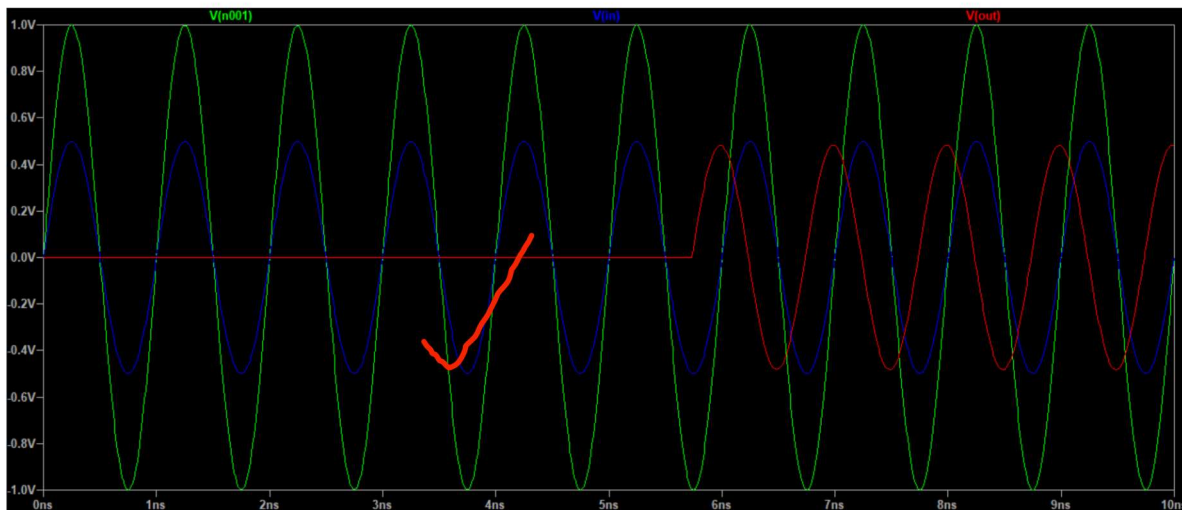6. Include the plot of their $v_{in}(t)$, $v_{out}(t)$ and $v_s(t)$ waveforms resulting from the LTspice simulation (single plot).



7. How does the magnitude of $v_{in}(t)$ compare to the magnitude $v_s(t)$?

At any point of the graph, $v_{in}(t)$ is about half of $v_s(t)$. For instance, when $v_s(t)$ is about 1V, $v_{in}(t)$ is 498.47V (about 500mV).

why?! -1

8. How does the magnitude $v_{out}(t)$ compare to the magnitude $v_{in}(t)$? Explain your observation.

It can be seen that $v_{out}(t)$ starts at about 5.8ns. Once $v_{out}(t)$ starts, a phase difference of about $\pi/2$ is observed. When either voltage is 0, it can be seen that the other is almost about to reach its max peak. This observation concludes a phase shift of $\pi/2$. It can also be seen that the peaks of both voltages are very close. While $v_{in}(t)$ is 498.47V, $v_{out}(t)$ is 482.98V which means that this is a low loss transmission line.

9. Calculate the attenuation constant α (in Np/m) of the TL using the peak values $v_{in}(t)$ $v_{out}(t)$ that you determined in Questions 7 and 8. Does this value agree with the value obtained with your MATLAB code?

calculate the attenuation constant of the TL using peaks of $V_{in}(t)$ & $V_{out}(t)$

peaks: $V_{in}(t) = 498.47 \text{ mV}$

$V_{out}(t) = 482.98 \text{ mV}$

$$\alpha = \ln \left(\frac{V_{in}(t)}{V_{out}(t)} \right)$$

$$= \ln \left(\frac{498.47 \text{ V}}{482.98 \text{ V}} \right)$$

$$\alpha = 0.03157$$

missing unit -1

The graph on MATLAB shows the attenuation constant to be just right above zero, therefore the calculated value (0.03157) agrees with the value from MATLAB.